

# QP Code 691 Electrical Circuit Theory.

APRIL 2024

PART-A

1) Ohm's Law :

It is defined as " At a constant Temperature the current flow through a conductor is directly proportional to the voltage between the two ends of the conductor.

$$V = IR.$$

2) Given ,

$$C = 100 \mu F$$

$$V = 500 V$$

TO Find :

$$E = ?$$


soln :

$$E = \frac{1}{2} V^2 \times C$$

$$E = \frac{1}{2} (500)^2 \times (100 \times 10^{-6})$$

$$E = 12.5 J.$$

3) Star / Delta Transformation :

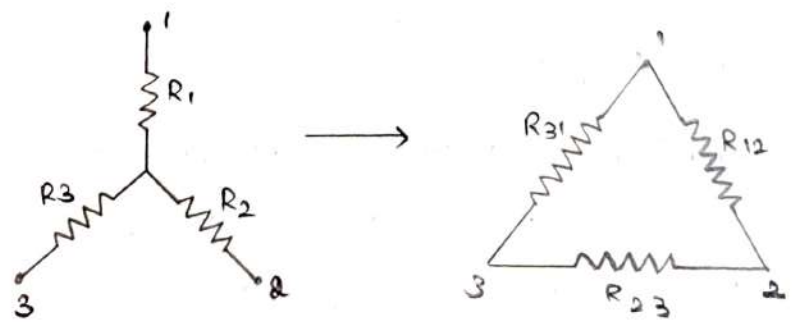


$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_{31} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

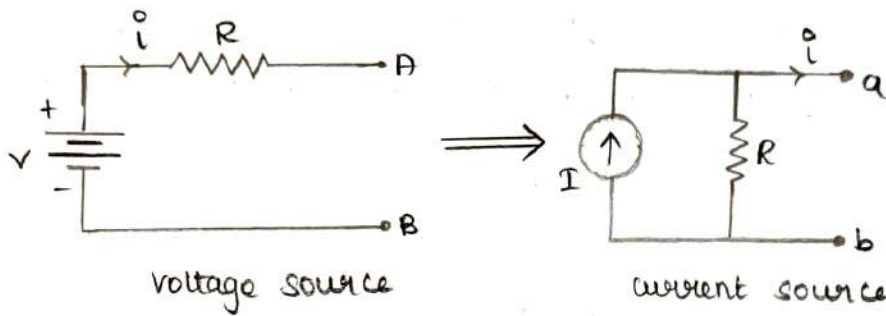4) Current equivalent of voltage source :



5) Average Value (or) Mean value :

The average value of all instantaneous values for a period of time .

$$I_{av} = \frac{i_1 + i_2 + i_3 + \dots + i_n}{n}$$

$$V_{av} = \frac{V_1 + V_2 + V_3 + \dots + V_n}{n}$$

$I_{av}$  (or)  $V_{av}$  for full cycle = 0 .

RMS Value (or) Effective value :

When an alternating current flow through a resistance for a certain time , certain amount of heat is produced .  
A steady DC current flows through the same

resistance for the same time same amount of heat is produced.

A steady DC current which has caused the same amount of heat is that of alternating current is called as RMS value.

$$I = \sqrt{\frac{i_1^2 + i_2^2 + i_3^2 + \dots + i_n^2}{n}}$$

$$V = \sqrt{\frac{V_1^2 + V_2^2 + V_3^2 + \dots + V_n^2}{n}}$$

b) i) Form factor:

The ratio of rms value to the average value of an alternating quantity is called form factor.

$$\text{Form factor} = \frac{\text{R.M.S value}}{\text{Average value}} = 1.1111$$


ii) Peak Factor:

The ratio of maximum value to the rms value to alternating quantity is called Peak factor.

$$\text{Peak Factor} = \frac{\text{maximum value}}{\text{RMS value}} = 1.414$$

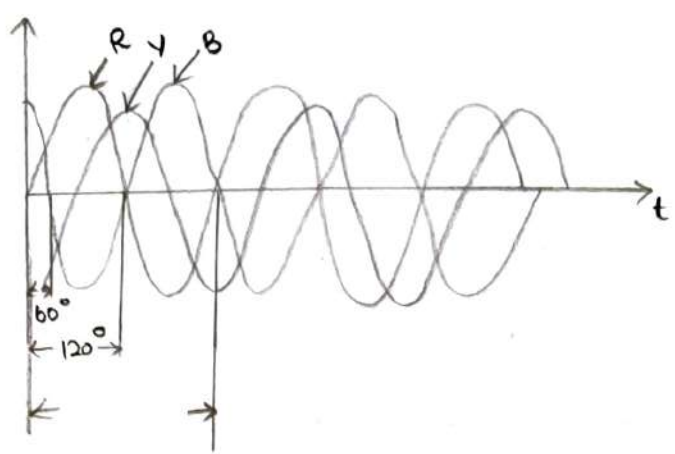
7) Phase Sequence:

The order in which the voltages in three phases reach their maximum value is called phase sequence. This is determined by a direction of rotation of alternator.



Positive Sequence = RYB

8)

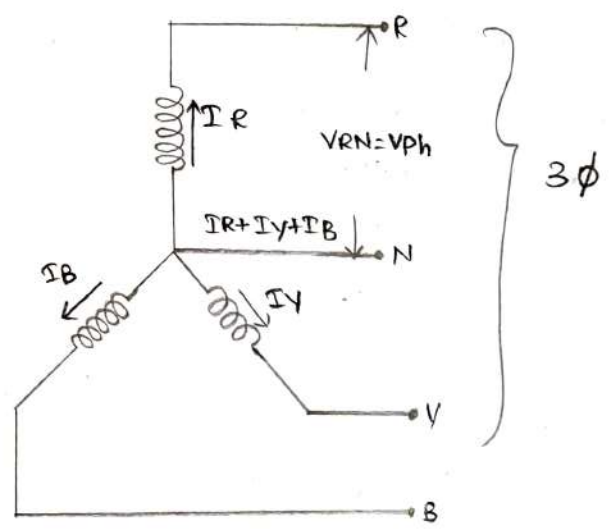

$$V_{RN} = V_{YN} = V_{BN} = V_{ph}$$

$$V_{RY} = V_{YB} = V_{BR} = V_L$$

In star connection,

$$I_L = I_{ph}$$

$$I_R = I_{RY} = I_B = I_{ph}$$

$$V_L \neq V_{ph}$$

$$I_L = I_{ph}$$

$$VRY^2 = VRN^2 + VYN^2 + 2VRN \cdot VYN \cos 60^\circ$$

$$= Vph^2 + Vph^2 + 2Vph \cdot Vph \cdot \frac{1}{2}$$

$$= Vph^2 + Vph^2 + Vph^2$$

$$VI^2 = 3Vph^2$$

$$VI = \sqrt{3Vph^2}$$

$$VI = \sqrt{3} Vph.$$

9) Active materials used in Nickel cadmium cell .

\* Nickel hydroxide  $Ni(OH)_2$  for the +ve plate exactly as in the nickel iron cell .

\* cadmium - (Cd) for -ve plate . The cadmium reduced in the internal resistance of the cell .

\* The electrolyte is potassium hydroxide (KOH), same as in the nickel - iron cell .

10) Ampere - hour efficiency :

It is the ratio of ampere - hour output to the ampere - hour input .


$$\text{Ampere efficiency} = \frac{\text{Ampere - hour output}}{\text{Ampere - hour input}} \times 100$$

$$= \frac{\text{Ampere - hours on discharge}}{\text{Ampere hours on charge}} \times 100 .$$

PART-B

11. a) i) Equivalent capacitance of 3 capacitors in series :

(MARKS : 4)

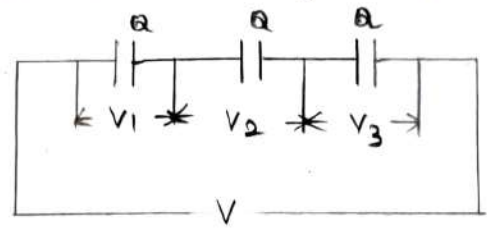

In series combination, charge on all capacitors is the same but pd across each is different.

$$\therefore V = V_1 + V_2 + V_3$$

$$\frac{Q}{C} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

(or)


$$C = \frac{C_1 C_2 C_3}{C_1 C_2 + C_2 C_3 + C_3 C_1}$$

Since,

$$Q = CV \Rightarrow V_1 = \frac{Q}{C_1}, V_2 = \frac{Q}{C_2}, V_3 = \frac{Q}{C_3}$$

where, C is total capacitance of the series combination.

ii)

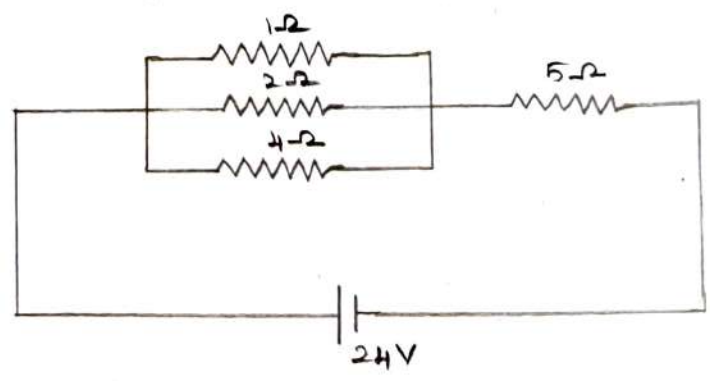

(CIRCUIT & CONSTRUCTION VALUE : (2))

Given,  
 $V = 24V$

Soln:

$$R_p = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} = \frac{1 \times 2 \times 4}{2 + 8 + 4} = \frac{8}{14} = 0.571 \Omega$$

$$R_{eq} = R_p + 5$$
$$= 5 + 0.571$$

$$R_{eq} = 5.571$$

(MARK: 2)

$$I = \frac{V}{R_{eq}} = \frac{24}{5.571} = 4.30A$$


(MARK: 1)

$$P = VI$$
$$= 24 \times 4.30$$

$$P = 103.2 \text{ Watts}$$

(MARK: 3)

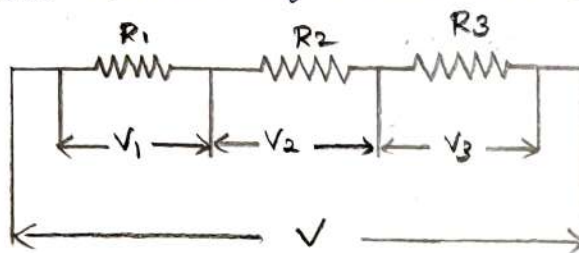11. B) i) Equivalent Resistance of 3 resistors in series:



(MARK: 4)

$$V = V_1 + V_2 + V_3$$


$$V_1 = IR_1 + IR_2 + IR_3$$

$$= I(R_1 + R_2 + R_3)$$

$$= R_1 + R_2 + R_3 \Rightarrow R = R_1 + R_2 + R_3$$

R is the total equivalent Resistance of the series circuit.

11)

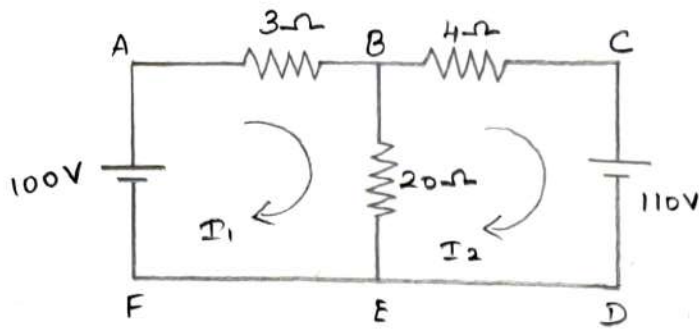

Branch current,

$AB = I_1$

$BC = I_2$

$BE = I_3$

Soln:

Loop ABFEA,

$$-3I_1 - 20(I_1 + I_2) + 100 = 0$$

$$-3I_1 - 20I_1 - 20I_2 + 100 = 0$$

$$(23I_1 + 20I_2) = 100$$

$$23I_1 + 20I_2 = 100 \rightarrow \textcircled{1}$$

Loop BCDEB,

$$4I_2 - 110 + 20(I_1 + I_2) = 0$$

$$4I_2 + 20I_1 + 20I_2 = 110$$

$$20I_1 + 24I_2 = 110 \rightarrow \textcircled{2}$$

$$23I_1 + 20I_2 = 100 \rightarrow \textcircled{1}$$

$$20I_1 + 24I_2 = 110 \rightarrow \textcircled{2}$$

eqn  $\textcircled{1}$   $\times 20$

$$460I_1 + 400I_2 = 2000$$

eqn  $\textcircled{2}$   $\times -23$

$$-460I_1 - 552I_2 = -2530$$

solve:  $460I_1 + 400I_2 = 2000$

$$-460I_1 - 552I_2 = -2530$$

---


$$-152I_2 = -530$$

(EACH

EQUATION)

(EACH MARK : (1))

STEPS AND ANSWER

MARK : (5)



$$I_2 = \frac{-530}{-152}$$

$$I_2 = 3.48 \text{ A}$$

sub  $I_2$  in eqn (1)

$$23 I_1 + 20(3.48) = 100$$

$$23 I_1 + 69.6 = 100$$

$$23 I_1 = 30.4$$

$$I_1 = \frac{30.4}{23}$$

$$I_1 = 1.32 \text{ A}$$

EACH BRANCH  
CURRENT: (3)

$$I_1 = \frac{\Delta I_1}{\Delta} = \frac{200}{152} = 1.315 \text{ A}$$

$$I_2 = 3.486, I_1 = 1.32 \text{ A}$$

$$I_2 = \frac{\Delta I_2}{\Delta} = \frac{530}{152} = 3.486 \text{ A}$$


$$I_3 = I_1 - I_2$$

$$= [1.315] - [3.486]$$

$$\text{Branch BE } (I_3) = -0.817 \text{ A}$$

Branch AB  $(I_1) = 1.315 \text{ A}$ , Branch BC  $(I_2) = 3.486 \text{ A}$

(A)  
(2) i)

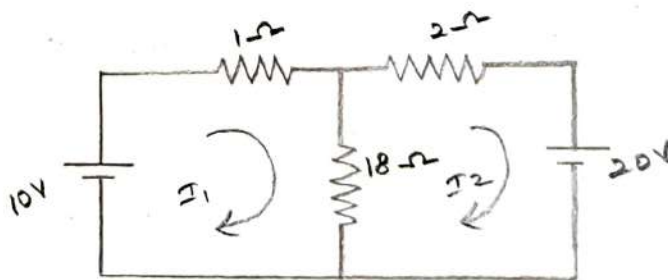

Soln:

$$\Delta = \begin{bmatrix} 19 & -18 \\ -18 & 20 \end{bmatrix} = (380) - (324)$$

Δ MARK: (2)

$$\Delta = 56$$

$$\Delta I_1 = \begin{bmatrix} 10 & -18 \\ -20 & 20 \end{bmatrix} = 200 - 360$$

$\Delta I_1$  MARK (2)

$$\Delta I_1 = -160$$

$$\Delta I_2 = \begin{bmatrix} 19 & 10 \\ -18 & 20 \end{bmatrix} = (-380) - (-180)$$

$$= -380 + 180$$

$$\Delta I_2 = -200$$

$\Delta I_2$  MARK : (2)

$$I_1 = \frac{\Delta I_1}{\Delta} = \frac{-160}{56} = -2.85 \text{ A}$$

$$I_2 = \frac{\Delta I_2}{\Delta} = \frac{-200}{56} = -3.57 \text{ A}$$

ANSWER : (A)


$$\begin{aligned} \therefore \text{Current flow through } 1\text{-}\Omega \text{ Resistor} &= I_1 - I_2 \\ &= 2.85 - (-3.57) \\ &= 2.85 + 3.57 \end{aligned}$$

$$\therefore I \text{ Through } 18\text{-}\Omega \text{ resistor} = 0.72 \text{ A}$$

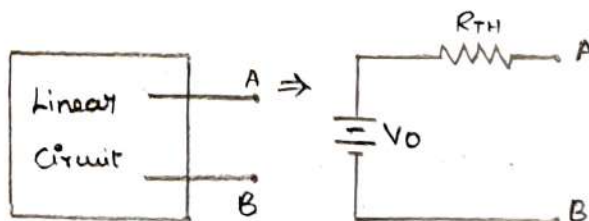(ii) Thevenin's Theorem :


MARK : (4)

A linear two terminal network can be replaced by a voltage source  $V_0$  in series with the resistance  $R_{TH}$ .




2) B) Superposition theorem:

MARK: (6)

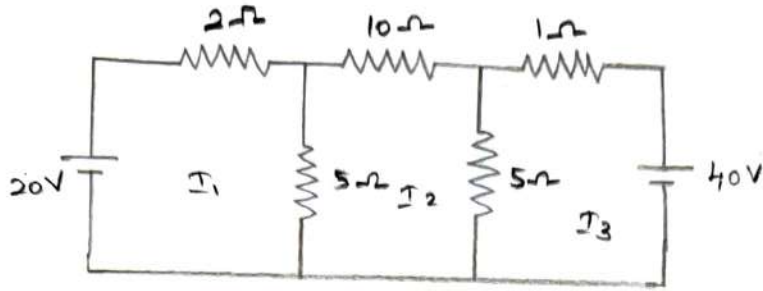

Case - I

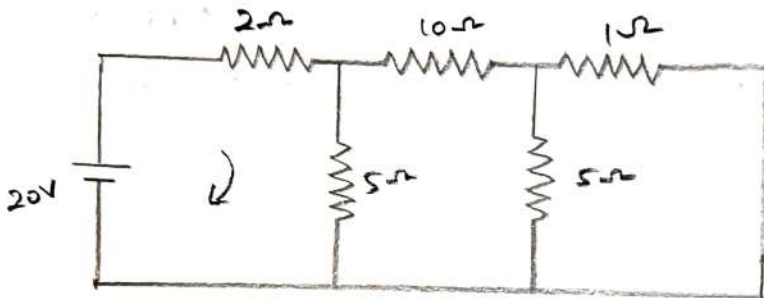20V source is active, 40V source is short circuited.



$$R = \begin{bmatrix} 7 & -5 & 0 \\ -5 & 20 & -5 \\ 0 & -5 & 6 \end{bmatrix} \quad V = \begin{bmatrix} 20 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 7 & -5 & 0 \\ -5 & 20 & -5 \\ 0 & -5 & 6 \end{bmatrix} = \begin{bmatrix} 7 & -5 & 0 & 7 & -5 \\ -5 & 20 & -5 & -5 & 6 \\ 0 & -5 & 6 & 0 & -5 \end{bmatrix}$$

$$= 840 - (175 + 150)$$

$$\Delta = 515$$

$$\Delta I_2 = \begin{bmatrix} 7 & 20 & 0 \\ -5 & 0 & -5 \\ 0 & 0 & 6 \end{bmatrix}$$

$$= \begin{bmatrix} 7 & 20 & 0 & 7 & 20 \\ -5 & 0 & -5 & -5 & 0 \\ 0 & 0 & 6 & 0 & 0 \end{bmatrix}$$

$$= -(-600)$$


$$\Delta I_2 = 600$$

$$I_2 = \frac{\Delta I_2}{\Delta} = 1.17A$$

Case - II

MARK: (6)

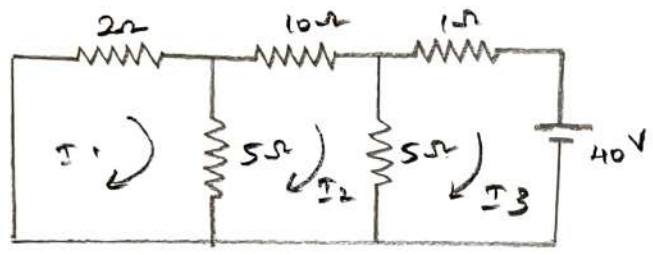40V source is Active, 20V source is short circuited.



$$R = \Delta = \begin{bmatrix} 7 & -5 & 0 \\ -5 & 20 & -5 \\ 0 & 5 & 6 \end{bmatrix} \quad V = \begin{bmatrix} 0 \\ 0 \\ -40 \end{bmatrix}$$

$$R = 515$$

$$\Delta I_2' = \begin{bmatrix} 7 & 0 & 0 \\ -5 & 0 & -5 \\ 0 & -40 & 6 \end{bmatrix} = \begin{bmatrix} 7 & 0 & 0 & 7 & 0 \\ -5 & 0 & -5 & -5 & 0 \\ 0 & -40 & 6 & 0 & -40 \end{bmatrix}$$

$$\Delta I_2' = 1400$$

$$I_2' = \frac{\Delta I_2'}{\Delta} = \frac{-1400}{515} = -2.72A$$


∴ Current flow through 10Ω resistor =  $I_2 + I_2'$

$$I_2 + I_2' = 1.17 + (-2.71)$$

$$= -1.55A$$

13.A)i)

(MARK : 6)

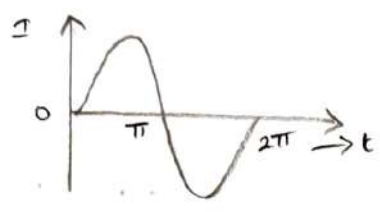

$$i = I_m \sin \theta$$

where,  $I_m$  is the maximum value

Average Value =  $\frac{\text{Area under the curve}}{\text{Base length}}$

$$I_{av} = \int_0^\pi \frac{I_m \sin \theta d\theta}{\pi}$$

$$= \frac{I_m}{\pi} [-\cos \theta]_0^\pi$$

$$= \frac{I_m}{\pi} [-(\cos \theta - \cos 0)]$$


$$= \frac{I_m}{\pi} [-(-1 - 1)]$$

$$= \frac{2I_m}{\pi} \text{ (or)}$$

$$I_{av} = 0.637 I_m$$

Similarly,  $V_{av} = 0.637 V_m$

ii)

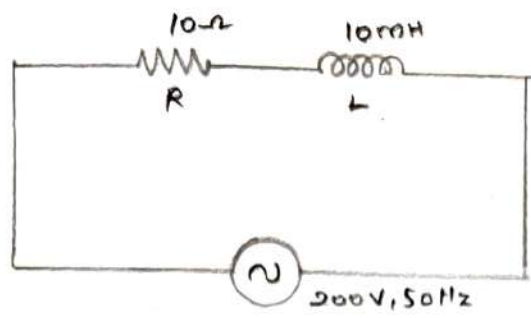

$$X_L = 2\pi fL$$

$$= 2 \times 3.14 \times 50 \times 10 \times 10^{-3}$$

$$X_L = 3.14$$

MARK: (2)

$$Z = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{10^2 + 3.14^2}$$

$$Z = 10.48 \Omega$$

MARK: (2)

$$I = V/Z$$

$$I = 200/10.48 = 19.08A$$

MARK: (2)

$$\phi = \cos^{-1} [R/Z]$$

$$= \cos^{-1} [10/10.48]$$

$$\cos \phi = 0.954$$

$$\phi = \cos^{-1} (0.954) = 17.24^\circ$$

MARK: (2)

13-B)

$$E = 100 \sin 314 t$$

$$E = E_m \sin \omega t$$

$$\omega t = 314 t, \quad \omega = 2\pi f$$

$$2\pi f = 314$$

$$f = \frac{314}{2\pi} = 49.97$$

MARK: (4)

$\therefore f = 50 \text{ Hz}$        $E_m = 100 \text{ volts}$

$$E_w = \frac{2 E_m}{\pi} = \frac{2 \times 100}{\pi}$$

$E_w = 63.66 \text{ volts}$       MARK : (1)

$$\text{RMS value} = \frac{E_m}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.72 \text{ volts}$$

$E_{\text{rms}} = 70.72 \text{ volts}$       MARK : (1)

$$E = 100 \sin 314 \left( \frac{1}{500} \right) = 99.99$$

MARK : (2)

$\therefore E = 100 \text{ volts}$  at time,  $t = \frac{1}{200}$  seconds

(H.A) 9)

A connection

Given

$$8 + j6, 230 \text{ V}$$

TO find,

$$I_t = ?$$

$$\cos \phi = ?$$

$$\text{Power} = ?$$

$$\text{volt ampere} = ?$$

Soln:

$$Z_{\text{ph}} = \sqrt{R^2 + X_L^2} = \sqrt{8^2 + 6^2} \quad Z_{\text{ph}} = 10.2$$

$$V_L = V_{\text{ph}} \text{ in } \Delta$$

$$V_L = V_{\text{ph}} = 230 \text{ V}$$

$$I_p = \frac{V_{\text{ph}}}{Z_{\text{ph}}} = \frac{230}{10} = 23 \text{ A}$$

$$I_L = \sqrt{3} I_{Ph}$$

$$= \sqrt{3} \times 23A$$

$$I_L = 39.83A$$

MARK : (3)

$$\cos\phi = \frac{R_P}{Z_{Ph}} = \frac{8}{10} = 0.8$$

$$\cos\phi = 0.8$$

MARK : (2)

$$Power = \sqrt{3} V_L I_L \cos\phi$$

$$= \sqrt{3} \times 230 \times 39.83 \times 0.8$$

$$P = 12693.71 \text{ watts}$$

MARK : (2)

$$\text{Volt ampere} = \sqrt{3} V_L I_L$$


$$= \sqrt{3} \times 230 \times 39.83$$

$$\text{Volt Ampere} = 15867.14 \text{ Volt ampere}$$

MARK : (3)

ii) 3 $\phi$  power measurement by two wattmeter method :

MARK : (4)

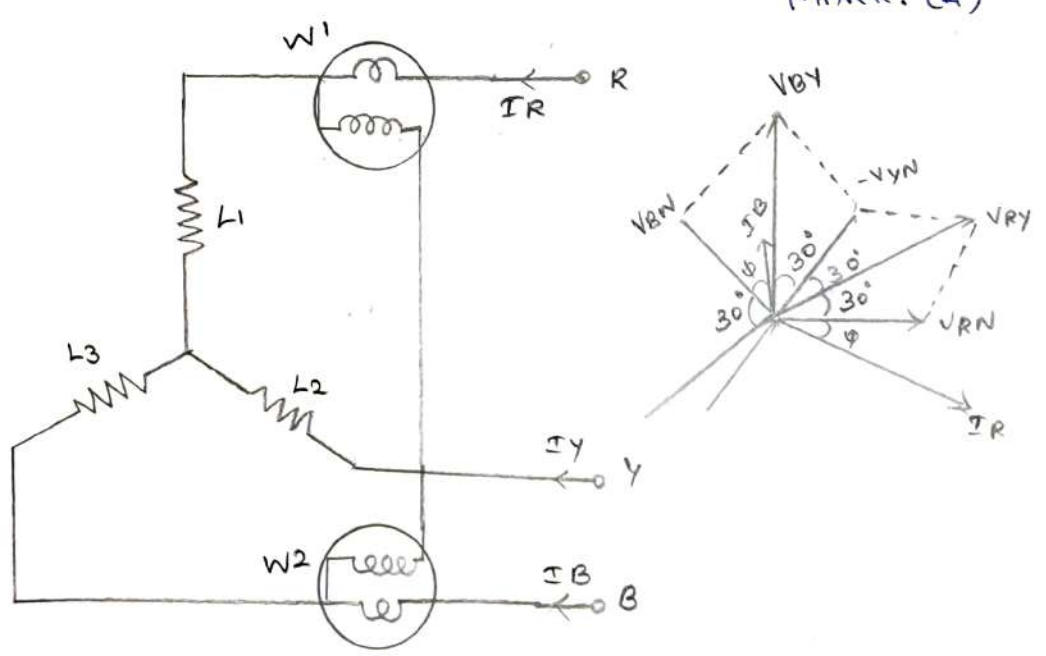



14. B) i)  $W_1 = 3000 \text{ W}$   
 $W_2 = 8000 \text{ W}$

To find,  
 Input power = ?  
 output power = ?

Soln:

Input power =  $W_1 + W_2$   
 $= 8000 + 3000$

Input power = 11000 Watts

MARK: (4)

$$\tan \phi = \sqrt{3} \left[ \frac{W_2 - W_1}{W_1 + W_2} \right]$$

$$= \sqrt{3} \left[ \frac{8000 - 3000}{3000 + 8000} \right]$$

$$= \sqrt{3} \left[ \frac{5000}{11000} \right]$$

$$= \sqrt{3} (0.4545)$$

$\tan \phi = 0.787$

$\phi = \tan^{-1}(0.787)$

$\phi = 38.20^\circ$      $\phi = 38.20^\circ$

Power factor =  $\cos \phi = \cos 38.20^\circ$

MARK: (6)

Power factor = 0.785

B ii) Positive Sequence :

MARK: (4)

In  $3\phi$  system, Positive sequence refers to the sequence of voltage or currents where the phase sequence is the same as the natural order (ABC).

### Negative sequence :

Negative sequence refers to a sequence where the phase sequence is reversed (CBA)

Positive sequence is characteristic of balanced operation while negative sequence can indicate unbalance or faults in the system.


### 15) A) Lead Acid Battery :

DIAGRAM 2

EXPLANATION MARK : (12)


A Battery consist of a number of cells and each cell of the battery consist of the following components :

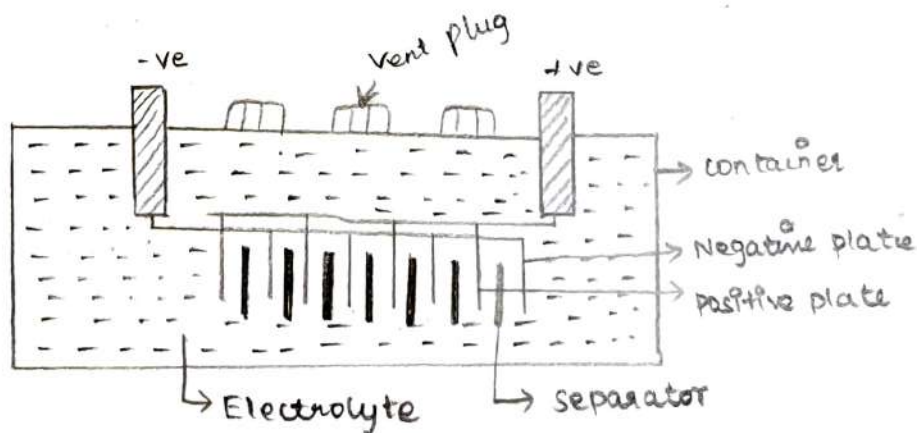- \* Container .
- \* Positive plate .
- \* negative plate .
- \* Separator .
- \* Electrolyte .
- \* Cell cover and vent plug .
- \* Cell connections .
- \* Battery Terminals .



Working :

Chemical Reaction During Discharging :

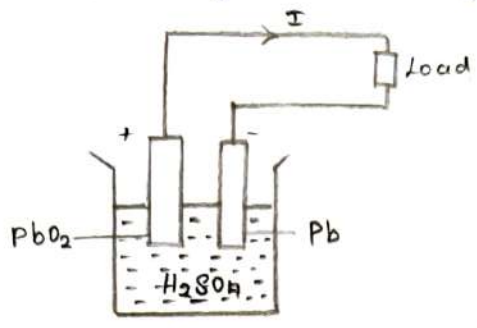


\* When the cell is fully charged its positive plate or anode is  $PbO_2$  which is dark chocolate brown in colour and the negative plate or cathode is  $Pb$  which is grey in colour.


\* During Discharging it stands current through the external load.

\* As the current within the cell is flowing from cathode to anode,  $H^+$  ions move towards the anode and  $SO_4$  ions move towards the cathode.


At Anode,

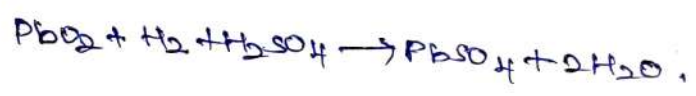

At Cathode,

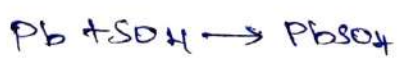

Chemical Reactions During charging :

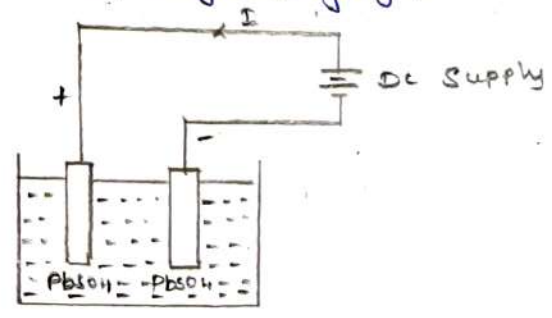


\* To recharge a discharged cell, direct current is passed through the cell in the reverse direction by connecting the anode to the +ve terminal of d.c.

\* During charging the  $H_2$  ions move towards the cathode and  $SO_4$  ions move towards the Anode.

Cathode  
At Cathode,



At Anode,

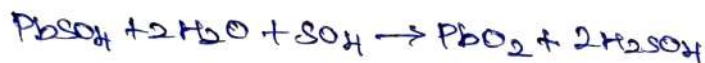

Application :

\* It is used in emergency lights in hospital and substations.

\* Used in Automobiles for starting and lighting

Purpose .

\* Used as power source in industries mines etc .

\* Used as power source for submarines .

\* Maintenance free batteries .

15) B) i) Care and maintenance of Batteries : (ANY 7

POINTS

MARK : (7))

\* Install the battery firmly .

\* Tighten all connections periodically .

\* Keep the battery dry and clear to avoid discharging

through moisture .

\* Keep the battery surface free of any electrolyte

\* Apply petroleum jelly to terminals to prevent

corrosion .

\* The level of the electrolyte must be kept above

the top of plate .


\* The cell should be recharged as soon as possible

after discharge .

\* Do not charge the battery at high rate .

ii) Mercury cells :

MARK : (7)

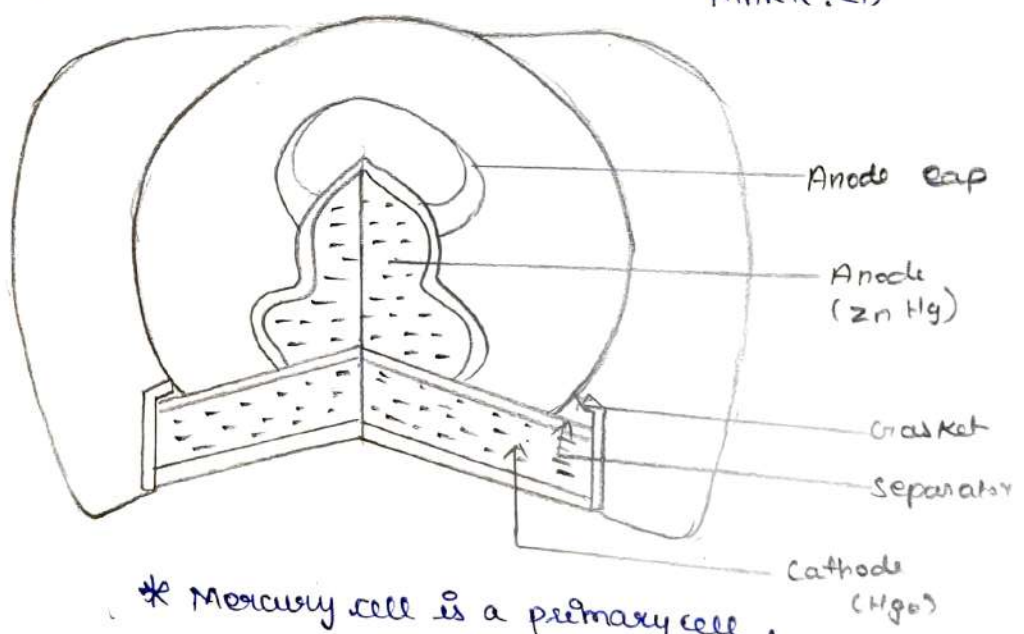

\* Mercury cell is a primary cell .

\* It can not be recharged and reused .

\* It is suitable for low current devices .

\* It is used in the shape of button cell for

hearing aids , watches , cameras etc . .

\* The cell produced about 1.35V .

Advantage :

- \* Low cost .
- \* Long life .

Dis advantage :

- \* It contained toxic mercury which pollute the environment .
- \* It cannot be recharged .

Prepared by,

M. A. Suresh Babu  
Lecturer (Sr. Sc) / EEE  
Thiagarajar Poly. College  
Salem.