

1317

## ELECTRICAL CIRCUIT THEORY

NOTE: Each Question carries 10 marks.

**1(a). Derive the equivalent resistance when three resistors are connected (i) in series (ii) in parallel.**

[Each - 5 marks]

### RESISTANCE IN SERIES:

- Resistances  $R_1$ ,  $R_2$ , and  $R_3$  are connected in series.
- Let  $V$  - be the applied voltage to the circuit  
 $I$  - be the total circuit current
- In a series circuit, the current through all resistors are same.
- Applied voltage is the sum of the individual voltage drops across each resistor.
- The total voltage across all three resistors is the sum of the voltage drops:

$$V = V_1 + V_2 + V_3 \text{----- (1)}$$

- Using Ohm's Law ( $V = IR$ ) for each resistor:
  - $V_1 = IR_1$        $V_2 = IR_2$        $V_3 = IR_3$

- Substituting in equation 1,  
 $V = IR_1 + IR_2 + IR_3$   
 $V = I (R_1 + R_2 + R_3)$   
 $V / I = R_1 + R_2 + R_3$


$$\mathbf{R = R_1 + R_2 + R_3 \ \Omega}$$

Where,  $R = V / I =$  Equivalent resistance


**Thus, the Equivalent resistance for three resistors in series is the sum of their individual resistances.**
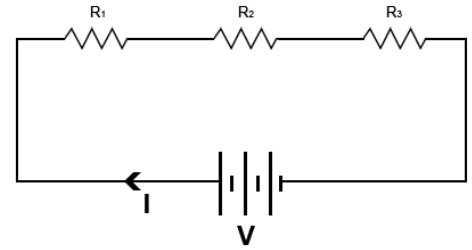
### RESISTANCE IN PARALLEL:

- Resistances  $R_1$ ,  $R_2$ , and  $R_3$  are connected in parallel.
- Let,  $V$  - be the applied voltage to the circuit  
 $I$  - be the total circuit current



*3 Resistors in series*

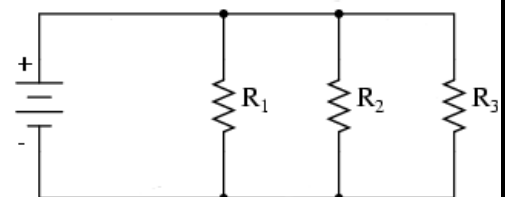

*3 Resistors in parallel*

- $I_1, I_2$  and  $I_3$  are the current through  $R_1, R_2$  and  $R_3$  respectively.
- **In parallel connection, the p.d. across all the resistors is the same but the current in each is different.**
- The total current in the circuit is the sum of currents flowing through each resistance.  
i.e.,  $I = I_1 + I_2 + I_3$  ----- (1)

- By Ohms law,  
 $I_1 = V / R_1, I_2 = V / R_2$  and  $I_3 = V / R_3$


- Substituting in equation 1,  
 $I = (V / R_1) + (V / R_2) + (V / R_3)$   
 $I = V [ (1/ R_1) + (1/ R_2) + (1/ R_3) ]$   
 $I / V = 1/R_1 + 1/R_2 + 1/R_3$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{eq} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

Where,  $R_{eq}$  is the equivalent resistance of parallel combination.

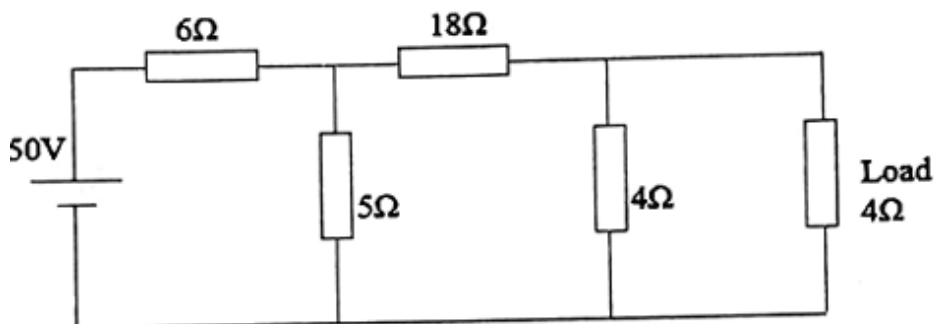**1(b). Find the current in the 4 Ω load resistor in the circuit shown below by mesh analysis.** **[10 marks]**




**SOLUTION:**

Let:

- $I_1$ : Current in Mesh 1.
- $I_2$ : Current in Mesh 2.
- $I_3$ : Current in Mesh 3.

Assuming Mesh currents,

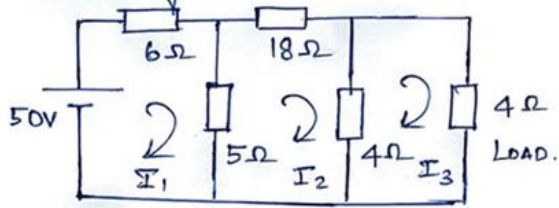

writing By Matrix form,

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} (6+5) & -5 & 0 \\ -5 & (5+18+4) & -4 \\ 0 & -4 & (4+4) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 11 & -5 & 0 \\ -5 & 27 & -4 \\ 0 & -4 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ 0 \end{bmatrix}$$

$$[R] \times [I] = [V]$$

$$\Delta = \begin{vmatrix} 11 & -5 & 0 \\ -5 & 27 & -4 \\ 0 & -4 & 8 \end{vmatrix} = 11[(27 \times 8) - (16)] - (-5)[-40 - 0] + 0[\quad] \\ = 11[216 - 16] + 5[-40] = 11 \times 200 - 200 = 10 \times 200$$

$$\Delta = 2000$$

$$\Delta_3 = \begin{vmatrix} +11 & -5 & 50 \\ -5 & 27 & 0 \\ 0 & -4 & 0 \end{vmatrix} = +50[20] = 1000 \Rightarrow \Delta_3 = 1000$$

Now,

$$\Delta = 2000$$

$$\Delta_3 = 1000$$


$$\text{Current } I_3 = \frac{\Delta_3}{\Delta} = \frac{1000}{2000} = 0.5 \text{ A.}$$

So, current through  $4\ \Omega$  Load Resistor,  $I_3 = 0.5 \text{ A.}$

**1(c). Derive an expression for delta to star transformation.**

**[10 marks]**

**SOLUTION:**

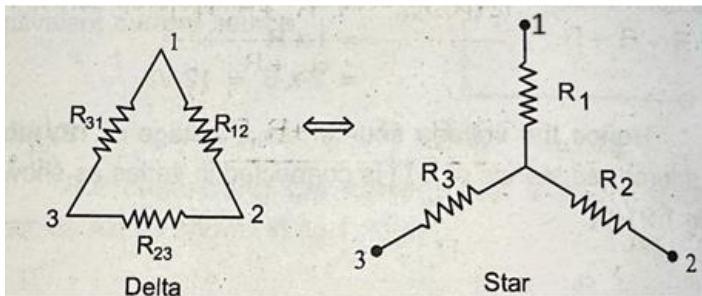

As shown in the figure, if the two systems are equivalent then the resistance between points 1 and 2 in delta and Resistance between points 1 and 2 in star are equal.

Resistance between terminals 1 and 2:

- In the  $\Delta$  network:

$$R_{12(\Delta)} = R_{12} + \frac{R_{31} \cdot R_{23}}{R_{31} + R_{23}}$$

- In the  $Y$  network:

$$R_{12(Y)} = R_1 + R_2$$

Equating the two:

$$R_1 + R_2 = R_{12} + \frac{R_{31} \cdot R_{23}}{R_{31} + R_{23}} \quad (1)$$

Resistance between terminals 2 and 3:

- In the  $\Delta$  network:

$$R_{23(\Delta)} = R_{23} + \frac{R_{12} \cdot R_{31}}{R_{12} + R_{31}}$$

- In the  $Y$  network:

$$R_{23(Y)} = R_2 + R_3$$

Equating the two:

$$R_2 + R_3 = R_{23} + \frac{R_{12} \cdot R_{31}}{R_{12} + R_{31}} \quad (2)$$

Resistance between terminals 3 and 1:

- In the  $\Delta$  network:

$$R_{31(\Delta)} = R_{31} + \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23}}$$

- In the  $Y$  network:

$$R_{31(Y)} = R_3 + R_1$$

Equating the two:

$$R_3 + R_1 = R_{31} + \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23}} \quad (3)$$

To find  $R_1$ :

Add Equations (1) and (3), then subtract Equation (2):

$$(R_1 + R_2) + (R_3 + R_1) - (R_2 + R_3) = \left( R_{12} + \frac{R_{31} \cdot R_{23}}{R_{31} + R_{23}} \right) + \left( R_{31} + \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23}} \right) - \left( R_{23} + \frac{R_{12} \cdot R_{31}}{R_{12} + R_{31}} \right)$$

Simplify to get:

$$R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

Similarly calculating  $R_2$  and  $R_3$ ,

$$R_2 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{23} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

**Final Delta-to-Star Transformation Equations:**


$$R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{23} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

**1(d). Using nodal analysis determine the current flowing through the 15  $\Omega$  resistor.**

**[10 marks]**

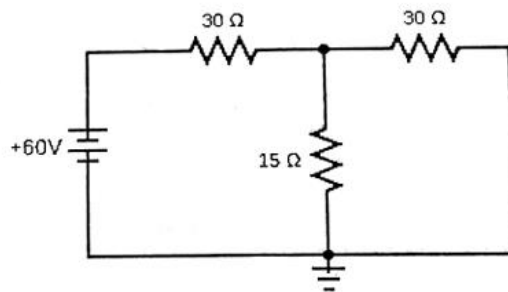


**SOLUTION:**

Let node be  $V_1$ .

Apply Kirchoff's Current Law (KCL) at Node  $V_1$ ,
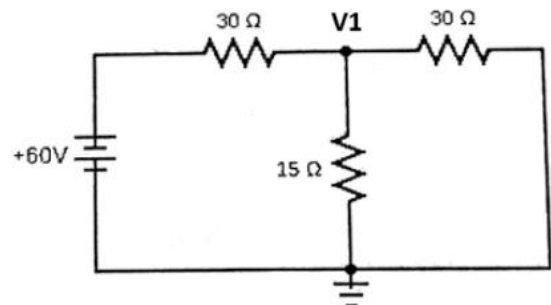
$$\frac{V_1 - 60}{30} + \frac{V_1}{15} + \frac{V_1}{30} = 0$$



$$\frac{V_1 - 60}{30} + \frac{2V_1}{30} + \frac{V_1}{30} = 0$$

$$\frac{4V_1 - 60}{30} = 0$$

$$4V_1 - 60 = 0$$

$$V_1 = 15 \text{ V}$$

The current through the  $15 \Omega$  resistor is given by:


$$I = \frac{V_1}{15}$$

Substituting  $V_1 = 15 \text{ V}$ ,

$$I = \frac{15}{15} = 1 \text{ A}$$

The current flowing through the  $15 \Omega$  resistor is:  $I = 1 \text{ A}$

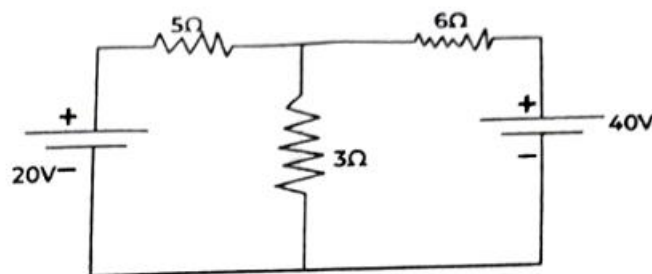**2(a). Using superposition theorem, find the current passing through the  $3\Omega$  resistor.**



To find the current passing through the  $3\Omega$  resistor using the **superposition theorem**, consider each source (one at a time) while replacing the other sources with their internal impedances:


- Voltage sources are replaced by short circuits (0 V)

**SOLUTION:**

[Step 1- 4 mark; Step 2- 4 marks; Step 3 – 2 marks]

STEP 1: short circuit 40V source.
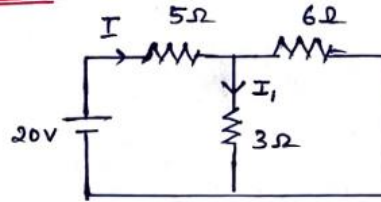
$$\Rightarrow I = \frac{20}{5 + \left[ \frac{6 \times 3}{6+3} \right]}$$
$$= \frac{20}{5 + \frac{18}{9}} = \frac{20}{5+2}$$




$$I = \frac{20}{7} \text{ A}$$

$$\Rightarrow I_1 = I \times \frac{6}{6+3} = \frac{20}{7} \times \frac{6}{9} = \frac{120}{63} = 1.90 \text{ A.}$$

$I_1 = 1.90 \text{ A}$   $\Rightarrow$  Current through  $3\Omega$  Resistor.  
because of 20V source.

STEP 2: short circuit 20V source:
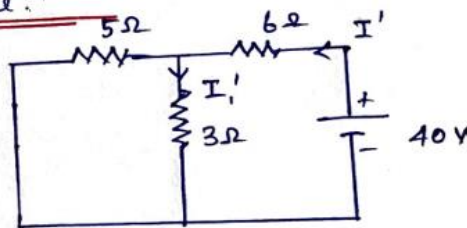
$$\Rightarrow I' = \frac{40}{6 + \left[ \frac{5 \times 3}{5+3} \right]} = \frac{40}{6 + \frac{15}{8}}$$
$$= \frac{40 \times 8}{48+15} = \frac{320}{63} = 5.07 \text{ A.}$$



$$\Rightarrow I_1' = I' \times \frac{5}{5+3} = \frac{5.07 \times 5}{8} = 3.168 \text{ A.}$$

$I_1' = 3.17 \text{ A}$   $\Rightarrow$  current through  $3\Omega$  Resistor because of  
40V source.



STEP 3: TOTAL CURRENT THROUGH 3Ω RESISTOR:

$$I_{\text{TOTAL}} = I_1 + I_1' = 1.9 + 3.17 = 5.07 \text{ A.}$$

$$I_{\text{TOTAL}} \approx 5 \text{ A.}$$


Total Current Through 3 Ω Resistor = 5 A

**2(b). State Norton's theorem. Also write its step-by-step procedure.**

[Statement - 4 marks, Procedure – 6 marks]

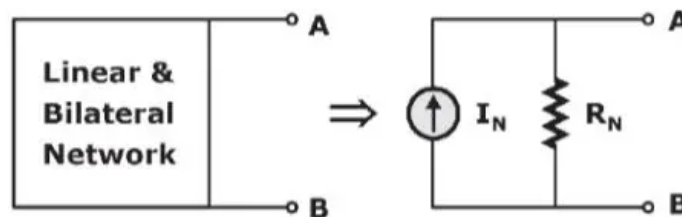**STATEMENT:**

Norton's theorem states that, any two terminal network can be reduced to a current source in parallel with a resistor.



NORTON'S EQUIVALENT CIRCUIT

Where,


- $I_N$  = Short Circuit current at terminals AB.
- $R_N$  = Equivalent Resistance of circuit from terminals AB.
- Load Current  $I_L = I_N \times [ R_N / (R_N + R_L) ]$

**Step by step procedure for finding Norton's Equivalent:**

1. Remove the load resistance and put a short circuit.
2. Find the short circuit current  $I_N$  or  $I_{SC}$ .
3. Replace all voltages with their internal resistance.
4. Find the Thevenin's looking back resistance of the network from the load terminals.
5. The current source  $I_N$  is joined in parallel with  $R_N$  between the two load terminals gives Norton's equivalent circuit.
6. Finally connect the load resistance.

$$\text{Load current } I_L = I_N \times [ R_N / (R_N + R_L) ].$$

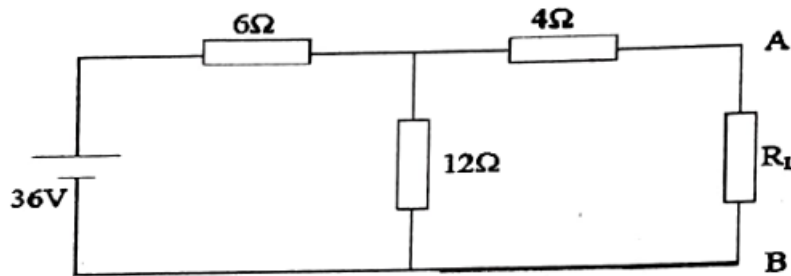**2(c). For the circuit shown below, find the value of  $R_L$  for which the maximum power is transferred from the source.** **[10 marks]**



**SOLUTION:**

Maximum power is transferred to the load resistor ( $R_L$ ) when its value is equal to the Thevenin resistance ( $R_{th}$ ) of the circuit as seen from the terminals A and B.

**Step 1: Simplify the Circuit to Find  $R_{th}$  :**

**1. Remove  $R_L$ :**

To find  $R_{th}$ , disconnect  $R_L$  and determine the equivalent resistance of the remaining circuit between terminals A and B.

**2. Simplify the Resistances:**

- The 6 Ω and 12 Ω resistors are in parallel:

$$R_{6||12} = \frac{6 \cdot 12}{6 + 12} = \frac{72}{18} = 4 \Omega$$

- The parallel combination ( $R_{6||12} = 4 \Omega$ ) is in series with the 4 Ω resistor:

$$R_{total} = R_{6||12} + 4 = 4 + 4 = 8 \Omega$$

**3. Thevenin Resistance:**

Thus, the Thevenin resistance ( $R_{th}$ ) is:

$$R_{th} = 8 \Omega$$

**Step 2: Maximum Power Transfer Condition**

For maximum power transfer, the load resistance  $R_L$  must equal the Thevenin resistance:

$$R_L = R_{th} \quad \text{i.e., } R_L = 8 \Omega$$


**2(d). Explain about Thevenin's theorem with an example.**

[Statement - 4 marks, Procedure – 6 marks]

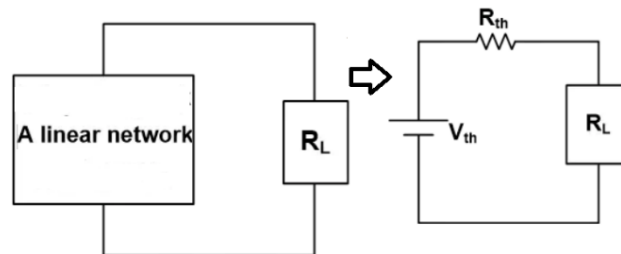**STATEMENT:**

A linear two terminal network can be replaced by a voltage source  $V_{th}$ , in series with the resistance  $R_{th}$  (or)

A linear circuit with two accessible terminals A and B can be reduced to a simple circuit as shown below.



*THEVENIN'S EQUIVALENT CIRCUIT*

Where,

$V_{th}$  is the open circuit voltage at terminals AB

$R_{th}$  is Thevenin's looking back resistance between terminals A and B.

**Step by step procedure for Thevenin's equivalent circuit;**

1. Remove the load whose current is required.
2. Find the open circuit voltage  $V_{th}$ , which is voltage across the two terminals where the load is removed.
3. All the voltage sources are replaced by their internal resistances.
4. Calculate the Thevenin's looking back resistance  $R_{th}$  from the two terminals.
5. Replace the entire network by the open circuit voltage  $V_{th}$  in series with the equivalent resistance  $R_{th}$ .
6. Connect the load resistance  $R$ , back to terminals A and B where it was already removed.
7. Then find the current flowing through  $R_L$

$$I = \frac{V_{th}}{(R_{th} + R_L)}$$

**3(a). Derive an expression for effective (RMS) value of sinusoidal wave in terms of its maximum value.** [Definition - 2 marks, Derivation – 8 marks]

**EFFECTIVE VALUE / ROOT MEAN SQUARE VALUE (RMS VALUE):**

- When an alternating current flows through a resistance for a certain time, a certain amount of heat is produced.
- The value of **direct current** when passed through the same resistance for the same time, which produces the same heat as that of alternating current is known as Root Mean Square value or Effective Value.

**RMS VALUE DERIVATION:**

Sinusoidal current,  $i = I_m \sin \Theta$

$$\text{R.M.S. value} = \sqrt{\frac{\text{Area of squared curve}}{\text{base}}}$$

$$I_{\text{RMS}} = \sqrt{\int_0^{\pi} \frac{(I_m \sin\theta)^2 d\theta}{\pi}} \quad \text{for half cycle}$$

$$= \sqrt{\frac{I_m^2}{\pi} \int_0^{\pi} \sin^2 \theta d\theta}$$

$$= \sqrt{\frac{I_m^2}{\pi} \int_0^{\pi} \frac{(1 - \cos 2\theta)}{2} d\theta}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \left[ \theta - \frac{\sin 2\theta}{2} \right]_0^{\pi}}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \left[ (\pi - 0) - \frac{(\sin 2\pi - \sin 0)}{2} \right]}$$

$$= \sqrt{\frac{I_m^2}{2\pi} (\pi - 0)} = \sqrt{\frac{I_m^2}{2}}$$

$I_{\text{RMS}} = I_m / \sqrt{2} = 0.707 I_m$  → Where,  $I_{\text{RMS}}$  is the RMS value of sinusoidal current.


Similarly,  $V_{\text{RMS}} = V_m / \sqrt{2} = 0.707 V_m$

**3(b). A coil of resistance 8 Ω, an inductance of 0.1H and a capacitance of 75 μfd is connected in series across a 230 V 50 Hz supply. Find (i) current in the circuit (ii)power factor.**

**SOLUTION:**

**Given Data:**

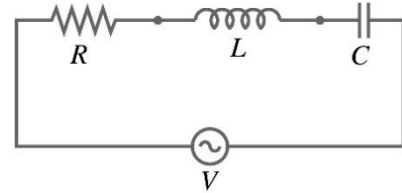1. Resistance  $R=8\ \Omega$
2. Inductance  $L =0.1\text{H}$
3. Capacitance  $C=75\ \mu\text{F}=75\times 10^{-6}\ \text{F}$
4. Voltage  $V=230\ \text{V}$
5. Frequency  $f= 50\text{Hz}$



**Angular frequency:**

$$\omega = 2\pi f = 2\pi(50) = 314.16\ \text{rad/s}$$

**Inductive Reactance ( $X_L$ ): [1 mark]**

$$X_L = \omega L = 2\pi f = 314.16 \times 0.1 = 31.416\ \Omega$$

**Capacitive Reactance ( $X_C$ ): [1 mark]**

$$X_C = 1 / \omega C = 1 / (2\pi f C) = 1 / (314.16 \times 75 \times 10^{-6}) = 1 / 0.023562 = 42.44\ \Omega$$

**Total Reactance:**

$$X = X_L - X_C = 31.416 - 42.44 = -11.024\ \Omega$$

**Impedance ( $Z$ ): [2 marks]**

$$Z = \sqrt{R^2 + X^2}$$

$$Z = \sqrt{8^2 + (-11.024)^2} = \sqrt{64 + 121.528} = \sqrt{185.528} = 13.62\ \Omega$$

**Current in the Circuit ( $I$ ): [3 marks]**

Using Ohm's law, the current is:  $I = V / Z = 230 / 13.62 = 16.89\ \text{A}$

**Power Factor (p.f.): [3 marks]**

$$\text{Power factor} = \cos \phi = R / Z = 8 / 13.628 = 0.587$$

**Final Answer:**


- (i) **Current in the circuit = 16.89 A**
- (ii) **Power factor = 0.587**

**3(c). A two element series circuit of  $R= 10\Omega$  and  $X_L=15\Omega$  has an effective voltage of 230 V at 50Hz. Determine the active power and apparent power.**

**SOLUTION:**

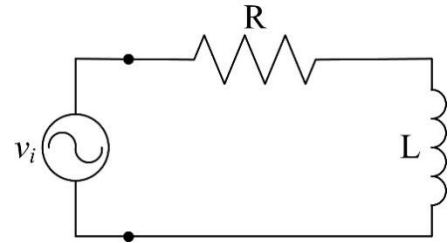**Given Data:**

- $R = 10 \Omega$
- $X_L = 15 \Omega$
- $V = 230 \text{ V}$
- $F = 50\text{Hz}$



**Impedance (Z): [2 marks]**

$$Z = \sqrt{R^2 + X^2}$$

$$Z = \sqrt{(10^2 + (15)^2)} = \sqrt{(100 + 225)} = \sqrt{325} = 18.03 \Omega$$

**Current (I): [1 mark]**

$$I = V / Z = 230 / 18.03 = 12.76 \text{ A}$$

**Power Factor (p.f.): [1 mark]**

$$\text{Power factor} = \cos \phi = R / Z$$

$$\cos \phi = 10 / 18.03 = 0.5547$$

**Active Power (P): [3 marks]**

$$P = V I \cos \phi$$

$$P = 230 \times 12.76 \times 0.5547 = 1633.5 \text{ W} = 1.63 \text{ KW}$$

**Apparent Power (S): [3 marks]**

$$S = VI$$

$$S = 230 \times 12.76 = 2934.8 \text{ VA} = 2.94 \text{ KVA}$$

**Final Answer:**

- Active Power = 1633.5 W = 1.63 KW**
- Apparent Power = 2934.8 VA = 2.94 KVA**

**3(d). Define the following terms: Form Factor, Peak factor, Impedance, Phase angle and Power factor.**

[Each Definition - 2 marks]

**FORM FACTOR:**

- The ratio of r.m.s. value to the average value of an alternating quantity is called form factor.
- Form factor = R.M.S. value / Average value = 1.11

**PEAK FACTOR:**

- The ratio of maximum value to the r.m.s. value of an alternating quantity is called peak factor.
- Peak factor = Maximum value / R.M.S. Value = 1.414

**IMPEDANCE (Z):**

- It is the opposition of flow of current when a.c voltage is applied to the circuit.
- It is also defined as the ratio of voltage and current flowing through the A.C circuit,  $Z = V / I$ .
- Its unit is Ohm  $\Omega$ .

**PHASE ANGLE ( $\phi$ ):**

- It is the angle between the voltage and current vector in an ac circuit.

**POWER FACTOR ( $\cos \phi$ ):**


- It is the cosine of the angle between the voltage and current.
- It is also defined as the ratio of true power (KW) to the apparent power (KVA) in a circuit.
- $\cos \phi = KW / KVA$ .

**4(a). Derive an expression for bandwidth in parallel resonance circuit.**


[Explanation - 3 marks; Diagram – 3 marks; Derivation – 4 marks]

- Bandwidth of the parallel resonance is the difference between the upper and lower cut off frequencies.
- Band width =  $f_2 - f_1$   
Where,
  - $f_2$  = Higher Cut off Frequency
  - $f_1$  = Lower Cut off Frequency
- $f_1$  and  $f_2$  are called half power points.
- Bandwidth of a circuit is defined as the frequencies lie between two points on either side of the resonant frequency where voltage is 0.707 of its maximum value.

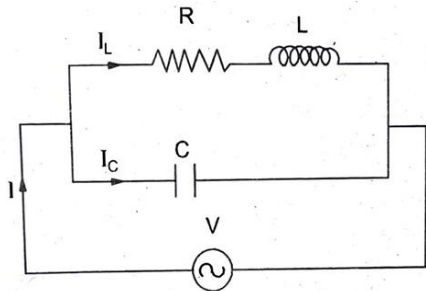- It is measured between the half power points. This corresponds to the 70.7% of voltage points since power is proportional to  $E^2$ .



Two Branch Parallel Resonant Circuit

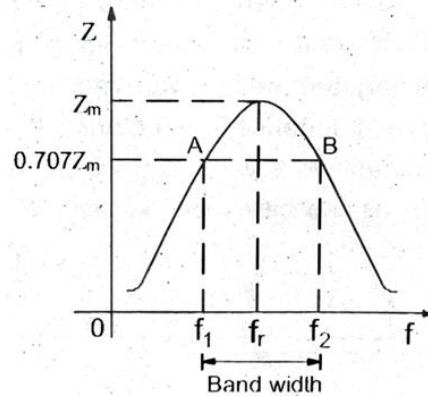

Resonance impedance diagram

### DERIVATION OF BANDWIDTH OF TWO BRANCH PARALLEL RESONANCE CIRCUIT:

$$\text{Quality factor (Q)} = \frac{\text{Resonant frequency}}{\text{Bandwidth}}$$

$$\text{i.e., } Q = \frac{f_r}{\text{BW}}$$

$$\Rightarrow \text{BW} = \frac{f_r}{Q}$$

$$\text{where, } Q = \text{factor} = \frac{\omega_r L}{R} = \frac{2\pi f_r L}{R}$$

$$\Rightarrow \text{BW} = \frac{f_r}{\frac{2\pi f_r L}{R}} = \frac{R}{2\pi L}$$

$$\Rightarrow \boxed{\text{BW} = \Delta f = \frac{R}{2\pi L}}$$

$$\because \omega = 2\pi f \Rightarrow \Delta\omega = 2\pi \Delta f$$

$$\Rightarrow \Delta\omega = \frac{R}{L}$$

Thus, BANDWIDTH of two branch parallel resonant circuit =  $R / L$




**4(b). Two impedances  $Z_1 = 10-j8$  Ohms and  $Z_2 = 7+j2$  Ohms are connected in parallel across 230V, 50Hz supply. Find the total impedance. [10 marks]**

**SOLUTION:**

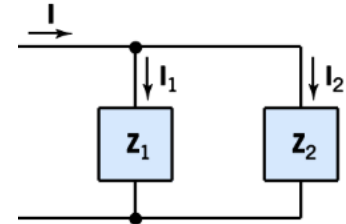**Given:**

- $Z_1 = 10-j8\Omega$
- $Z_2 = 7+j2 \Omega$



When two impedances  $Z_1$  and  $Z_2$  are connected in parallel, Total Impedance  $Z_{\text{Total}}$  is,

$$\frac{1}{Z_{\text{total}}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

**Calculating reciprocal of each impedance:**

The reciprocal of an impedance  $Z=R+jX$  is :

$$\frac{1}{Z} = \frac{1}{R + jX} = \frac{R - jX}{R^2 + X^2}$$

For  $Z_1 = 10 - j8$ :

$$\frac{1}{Z_1} = \frac{10 + j8}{10^2 + (-8)^2} = \frac{10 + j8}{100 + 64} = \frac{10 + j8}{164}$$
$$\frac{1}{Z_1} = 0.06098 + j0.04878 \Omega^{-1}$$

For  $Z_2 = 7 + j2$ :

$$\frac{1}{Z_2} = \frac{7 - j2}{7^2 + 2^2} = \frac{7 - j2}{49 + 4} = \frac{7 - j2}{53}$$
$$\frac{1}{Z_2} = 0.13208 - j0.03774 \Omega^{-1}$$

**Adding the reciprocals:**

$$\frac{1}{Z_{\text{total}}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\frac{1}{Z_{\text{total}}} = (0.06098 + j0.04878) + (0.13208 - j0.03774)$$

$$\frac{1}{Z_{\text{total}}} = (0.06098 + 0.13208) + j(0.04878 - 0.03774)$$

$$\frac{1}{Z_{\text{total}}} = 0.19306 + j0.01104 \Omega^{-1}$$

**Calculating  $Z_{\text{Total}}$ :**

$$Z_{\text{total}} = \frac{1}{0.19306 + j0.01104}$$

Multiply numerator and denominator by the conjugate of the denominator:

$$Z_{\text{total}} = \frac{1}{0.19306 + j0.01104} \cdot \frac{0.19306 - j0.01104}{0.19306 - j0.01104}$$

$$Z_{\text{total}} = \frac{0.19306 - j0.01104}{(0.19306)^2 + (0.01104)^2}$$

$$Z_{\text{total}} = \frac{0.19306 - j0.01104}{0.03725 + 0.00012}$$

$$Z_{\text{total}} = \frac{0.19306 - j0.01104}{0.03737}$$

$$Z_{\text{total}} = 5.17 - j0.30 \Omega$$

**Final Answer:**

**The total impedance is:**

$$Z_{\text{Total}} = 5.17 - j0.30 \Omega$$

**4(c). Derive expressions for half power frequencies in series resonant circuit.**

[Diagram – 2 marks; Derivation – 8 marks]

- At half power frequencies or cut-off frequencies the power will be equal to half the power at resonance.
- Current in the Circuit:

$$I = \frac{V}{|Z|} = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

- The power dissipated in the resistor is:

$$P = I^2 R = \frac{V^2}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} R \quad \text{----- (1)}$$

- Power at resonance:  $P_R = V^2 / R$  -----(2)

- At Half power Frequency:

$$P = P_R / 2 \quad \text{-----(3)}$$

- Substitute (1) & (2) in (3),

$$\frac{V^2}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} R = \frac{V^2}{2R}$$


$$R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2 = 2R^2$$

$$\left(\omega L - \frac{1}{\omega C}\right)^2 = R^2$$

$$\omega L - \frac{1}{\omega C} = \pm R$$

⇒ Multiply By  $\omega C$ ,

$$\omega^2 LC - 1 = \pm \omega RC$$

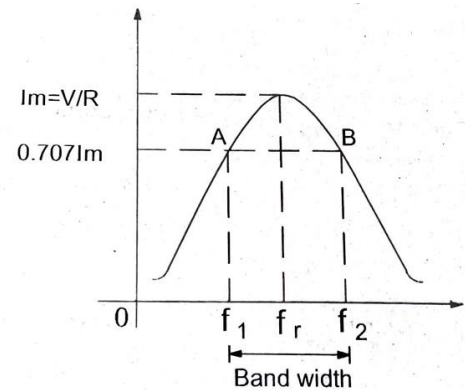

Series Resonance Curve

⇒ Divide By LC,

$$\omega^2 - \frac{1}{LC} = \pm \frac{\omega R}{L}$$
$$\omega^2 + \frac{\omega R}{L} - \frac{1}{LC} = 0$$

⇒ Solving the above quadratic equation, we get two roots,

$$1. \quad \omega = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$2. \quad \omega = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

- The half power frequency or cut-off frequencies are given by the positive roots of the quadratic equation

- **Higher Cut off Frequency:**

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

- **Lower Cut Off Frequency:**

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

- $\omega = 2\pi f$  gives,

$$f_2 = \frac{\omega_2}{2\pi} = \frac{1}{2\pi} \left[ \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right]$$

$$f_1 = \frac{\omega_1}{2\pi} = \frac{1}{2\pi} \left[ -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right]$$

Where, **f1** and **f2** are half power frequencies in series resonant circuit

**4(d). Discuss about the effects of varying inductance and capacitance in series RLC circuit.** [Each 5 marks]

**EFFECTS OF VARYING INDUCTANCE:**

- When a constant voltage, constant frequency source is applied across a series RLC circuit with inductance varied,  $X_C$  will be constant.
- The value of  $X_L$  increases directly with the value of  $L$  ( $X_L = 2 \pi f L$ ).
- When the inductance is zero, the current is limited by  $R$  and  $C$  ( $Z = \sqrt{R^2 + X_C^2}$ ).
- As  $X_L$  increases the effective reactance ( $X_L - X_C$ ) reduces and the current increases.
- At  $X_L = X_C$  the current is limited only by the resistance of the circuit and the current is maximum equal to  $(V/R)$ . This is the resonance condition.
- Further increasing of  $L$ , the impedance of the circuit increases and the current decreases.
- When  $L$  approached infinity the current falls to zero.

**EFFECTS OF VARYING CAPACITANCE:**

- When a series R.L.C circuit with constant frequency constant voltage source is applied across a RLC series circuit with capacitance alone varied and  $X_L$  is constant.
- $X_C$  varies inversely with the value of  $C$ . When  $C$  is very small,  $X_C$  is very large, and the current is very small.
- As  $C$  increased,  $X_C$  decreases, when  $X_C = X_L$ , the current is limited, only by  $R$  and the current is maximum. This is the resonance condition.
- As  $C$  approaches infinity,  $X_C$  is equal to zero and the current is limited by  $R$  and  $L$ .

**5(a). A balanced delta connected load of  $4+j8$  Ohms per phase is connected to a 3 phase 400V supply. Find the line current, power and total volt ampere.**

**SOLUTION:**

**Given Data:**

- Load impedance per phase:  $Z_{ph} = 4+j8 \Omega$
- Supply voltage:  $V_L = 400 V$


**Phase Voltage:**

For Delta connected load,  $V_{ph} = V_L = 400V$

**Impedance: [1 mark]**

$$|Z_{ph}| = \sqrt{R^2 + X^2}$$

$$|Z_{ph}| = \sqrt{4^2 + (8)^2} = \sqrt{16 + 64} = \sqrt{80} = 8.944 \Omega$$

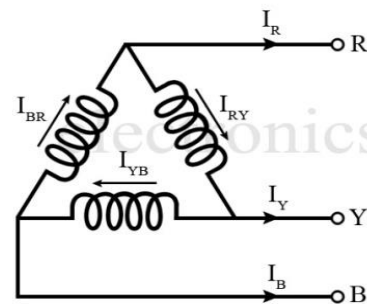

**Power Factor:**

$$\cos \phi = R / Z = 4 / 8.944 = 0.4472$$

**Phase Current:**

$$I_{Ph} = V_{ph} / |Z_{ph}| = 400 / 8.944 = 44.72 \text{ A}$$

**Line Current:** [3 marks]

$$I_L = \sqrt{3} I_{Ph} = \sqrt{3} \times 44.72 = 77.49 \text{ A}$$

**Active Power (P):** [3 marks]

The active power is given by:

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$P = \sqrt{3} \times 400 \times 77.49 \times 0.4472 = 24001.0 \text{ W} = 24 \text{ kW}$$

**Volt Ampere or Apparent Power (S):** [3 marks]

$$S = \sqrt{3} V_L I_L$$

$$S = \sqrt{3} \times 400 \times 77.49 = 53,686.6 \text{ VA} = 53.69 \text{ kVA}$$

**Final Results:**

- **Line Current:**  $I_L = 77.49 \text{ A}$
- **Power (P):** 24 kW
- **Total Volt Ampere (S):** 53.69 kVA

**5(b). A three phase 440 V load operates with a power factor of 0.7. The total power taken from the mains is 60kW. Two-Watt meters are connected to measure the input power. Find the readings of each Wattmeter. [10 marks]**

**SOLUTION:**

**Given Data:**

- Line voltage = 440V
- Total power (P) = 60 kW
- Power factor ( $\cos\phi$ ): 0.7

**Phase angle  $\phi$ :** [2 marks]

$$\cos\phi = 0.7 \Rightarrow \phi = \cos^{-1}(0.7) = 45.57^\circ$$

**Line current  $I_{\text{line}}$ :** [2 marks]

$$P = \sqrt{3} V_{\text{line}} \cdot I_{\text{line}} \cdot \cos\phi$$

$$I_{\text{line}} = \frac{P}{\sqrt{3} \cdot V_{\text{line}} \cdot \cos\phi}$$

$$I_{\text{line}} = \frac{60,000}{\sqrt{3} \cdot 440 \cdot 0.7} = \frac{60,000}{533.4} = 112.47 \text{ A}$$

**Wattmeter Readings:** [6 marks]

The readings of the two wattmeters ( $W_1$  and  $W_2$ ) in a three-phase system are given by:

$$W_1 = V_{\text{line}} \cdot I_{\text{line}} \cdot \cos(30^\circ - \phi)$$

$$W_2 = V_{\text{line}} \cdot I_{\text{line}} \cdot \cos(30^\circ + \phi)$$

Calculate  $W_1$ :

$$W_1 = 440 \cdot 112.47 \cdot \cos(30^\circ - 45.57^\circ)$$

$$W_1 = 440 \cdot 112.47 \cdot \cos(-15.57^\circ) = 440 \cdot 112.47 \cdot 0.9659$$

$$W_1 = 47,799.3 \text{ W or } 47.8 \text{ kW}$$

Calculate  $W_2$ :

$$W_2 = 440 \cdot 112.47 \cdot \cos(30^\circ + 45.57^\circ)$$

$$W_2 = 440 \cdot 112.47 \cdot \cos(75.57^\circ) = 440 \cdot 112.47 \cdot 0.2588$$

$$W_2 = 12,799.2 \text{ W or } 12.8 \text{ kW}$$

**Final Results:**

- **Wattmeter 1 Reading ( $W_1$ ): 47.8 kW**
- **Wattmeter 2 Reading ( $W_2$ ): 12.8 kW**

Note: This can also be solved by any other method.

**5(c). Discuss about delta connected unbalanced loads.**

[Diagram - 2 marks; Explanation – 8 marks]

- Figure shows an unbalanced delta connected load.
- Assume a phase sequence of RYB.
- The unbalanced delta connected load supplied from a balanced 3 phase supply does not present any new problems because the voltage across the load phase is fixed.
- It is independent of the nature of the load.
- For delta connection line voltage is equal to phase voltage.
- Taking  $V_{RY}$  as the reference phasor. Assuming the phase sequence is RYB.

**Line or Phase Voltages are:**

$$\therefore V_{RY} = V \angle 0^\circ \text{ V}$$

$$V_{YB} = V \angle -120^\circ \text{ V}$$

$$V_{BR} = V \angle -240^\circ \text{ V}$$

**Phase Currents are:**

$$I_{RY} = \frac{V_{RY}}{Z_{RY}} = \frac{V \angle 0^\circ}{Z_1 \angle \phi_1^\circ}$$

$$I_{YB} = \frac{V_{YB}}{Z_{YB}} = \frac{V \angle -120^\circ}{Z_2 \angle \phi_2^\circ}$$

$$I_{BR} = \frac{V_{BR}}{Z_{BR}} = \frac{V \angle -240^\circ}{Z_3 \angle \phi_3^\circ}$$


**Line Currents are:**

$$I_R + I_{BR} = I_{RY}$$

**Thus,  $I_R = I_{RY} - I_{BR}$**

**Similarly,  $I_Y = I_{YB} - I_{RY}$**

$$I_B = I_{BR} - I_{YB}$$

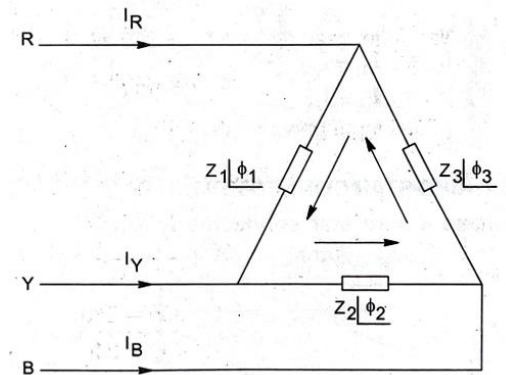


*Delta Connected Load*



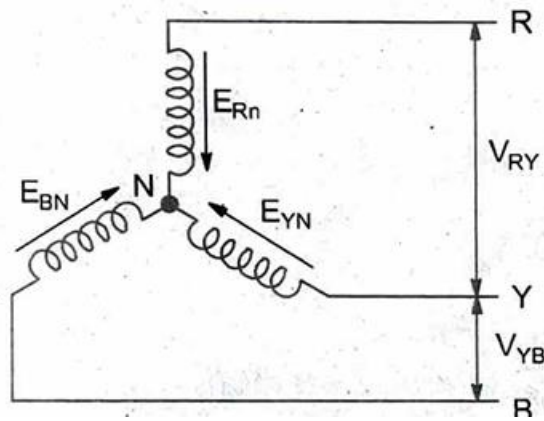
**5(d). Derive the relation between voltages and currents of line and phase values in star connected systems.**

[Diagram - 4 marks; Derivation – 6 marks]

- Below figure shows a balanced 3 phase Y-connected system.
- The e.m.f. generated in the three phases are  $E_{RN}$ ,  $E_{YN}$  and  $E_{BN}$  are equal in magnitude but displaced  $120^\circ$  from one another.
  - i.e.,  $E_{RN} = E_{YN} = E_{BN} = V_{ph}$
  - $V_{ph}$  = Phase voltage i.e., voltage between phase and Neutral
  - $V_{RY} = V_{YB} = V_{BR} = V_L$
  - $V_L$  = Line voltage i.e., voltage between two lines.



Star Connected System

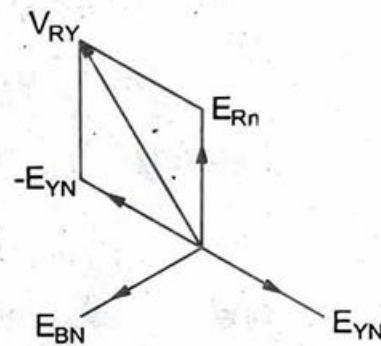

Vector Diagram

From the figure

$$V_{RY} = E_{RN} + E_{NY} \text{ ----- (Phasor sum)}$$

$$V_{RY} = E_{RN} - E_{YN} \text{ ----- (Phasor difference)}$$

From the vector diagram shown in figure,

$$\begin{aligned} V_{RY} &= \sqrt{E_{RN}^2 + E_{YN}^2 + 2E_{RN} E_{YN} \cos 60} \\ &= \sqrt{V_{ph}^2 + V_{ph}^2 + 2 V_{ph} V_{ph} \times 1/2} \\ &= \sqrt{3} V_{ph}^2 \\ &= \sqrt{3} V_{ph} \end{aligned}$$

Similarly,

$$V_{YB} = E_{YN} - E_{BN} = \sqrt{3} V_{Ph}$$


**Hence in a balanced 3 phase star connection Line Voltage  $V_L = \sqrt{3} V_{ph}$ .**

**Line Current and Phase Current:**

- In Y - connection each line conductor is connected in series to a separate phase as shown in figure. Therefore, line current is equal to phase current.

**In Star Connection i.e.,  $I_L = I_{Ph}$**

Prepared by,

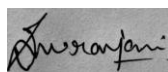

Mrs. Manoranjani M,

Lecturer/EEE,

149, Government Polytechnic College,

Vanavasi, Salem-636457.